

22. **REASONING** The average power dissipated is that dissipated in the resistor and is $\bar{P} = I_{\text{rms}}^2 R$, according to Equation 20.15b. We are given the current I_{rms} but need to find the resistance R . Since the inductive reactance X_L is known, we can find the resistance from the impedance, which is $Z = \sqrt{R^2 + X_L^2}$, according to Equation 23.7. Since the voltage and the current are known, we can obtain the impedance from Equation 23.6 as $Z = V_{\text{rms}}/I_{\text{rms}}$.

SOLUTION From Equation 23.7, we can determine the resistance as $R = \sqrt{Z^2 - X_L^2}$. With this expression for the resistance, Equation 20.15b for the power becomes

$$\bar{P} = I_{\text{rms}}^2 R = I_{\text{rms}}^2 \sqrt{Z^2 - X_L^2}$$

Using Equation 23.6 to express the impedance, we obtain the following value for the dissipated power

$$\begin{aligned}\bar{P} &= I_{\text{rms}}^2 \sqrt{Z^2 - X_L^2} = I_{\text{rms}}^2 \sqrt{\left(\frac{V_{\text{rms}}}{I_{\text{rms}}}\right)^2 - X_L^2} \\ &= (1.75 \text{ A})^2 \sqrt{\left(\frac{115 \text{ V}}{1.75 \text{ A}}\right)^2 - (52.0 \text{ } \Omega)^2} = \boxed{123 \text{ W}}\end{aligned}$$