

49. **REASONING AND SOLUTION**

a. Equation 20.14 gives

$$I = \frac{V}{R} = \frac{120 \text{ V}}{240 \Omega} = \boxed{0.50 \text{ A}}$$

b. Since there is no inductor, Equations 23.6 and 23.7 apply with  $X_L = 0 \Omega$ . Therefore, the current is  $I = V/Z = V/\sqrt{R^2 + X_C^2}$ . Using Equation 23.2 for  $X_C$ , we find

$$I = \frac{V}{\sqrt{R^2 + \left(\frac{1}{2\pi f C}\right)^2}} = \frac{120 \text{ V}}{\sqrt{(240 \Omega)^2 + \left[\frac{1}{2\pi(60.0 \text{ Hz})(10.0 \times 10^{-6} \text{ F})}\right]^2}} = \boxed{0.34 \text{ A}}$$

c. When an inductor is present, Equations 23.6 and 23.7 give the current as  $I = V/Z = V/\sqrt{R^2 + (X_L - X_C)^2}$ . This expression reduces to  $I = V/R$  when  $X_L = X_C$ . Using Equations 23.2 and 23.4 for the reactances, we find that

$$2\pi f L = \frac{1}{2\pi f C} \quad \text{or} \quad L = \frac{1}{4\pi^2 f^2 C} = \frac{1}{4\pi^2 (60.0 \text{ Hz})^2 (10.0 \times 10^{-6} \text{ F})} = \boxed{0.704 \text{ H}}$$

Yes, it is possible to return the current to the value calculated in part (a).